

Part 0 - Prerequisites

Required software

- Windows
 - Microchip Studio (Optionally: MPLAB X)
- Mac OS/Linux
 - MPLAB X
- All OS
 - TeraTerm (Optionally: PuTTY, other serial COM interface)
 - Only AVR is required, other devices can be ignored (unchecked) during installment
 - SAM
 - PIC
 - UC3
 - dsPIC
 - etc

Basic Electronics

- A refresher for those who have been out of the game for a while
- An introduction to the uninitiated
- Not a comprehensive guide!
 - If nothing makes sense, go online and learn more!
 - Keywords
 - Kirchoff's laws
 - Ohm's law
 - Introduction to electronics
 - Try GPT UiO?
 - GPT is a good tool to be introduced to a topic
 - But some things are still best learnt the "hard way"

Electrical Circuits


- Flow of current and electric potentials can be used to do useful things
 - Analogy: Liquids in pipes and plumbing
 - Electric potential – Pressure
 - Current – Flow
- Maxwell's laws
 - A time varying magnetic field gives rise to electric fields, and vice versa
 - Electric fields – Potential difference
 - Monopoles exist – Free charges
 - Magnetic fields – Current flow
 - Monopoles do not exist
- Fields beyond scope of introduction
 - Potential is measured in Volts [V] between two points
 - Current is measured in Ampere [A] in cross-section

Passive Components

- Resistor
 - Restricts current flow
 - Real component – induces losses
- Capacitor
 - Stores energy in the form of electric fields
 - Lossless (in theory)
- Inductor
 - Stores energy in the form of magnetic fields
 - Lossless (in theory)


Resistor

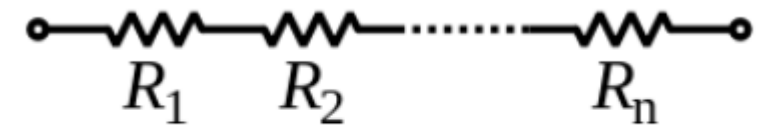- Value of a resistor is measured in Ohms [Ω]
- Energy dissipated as heat
 - $P = V * I$
 - Power = Voltage * Current
- Ohms law
 - $V = I * R$
 - Voltage = Current * Resistance
- Equivalent series resistance
 - Sum of resistor values
- Equivalent parallel resistance
 - Inverse sum of inverse resistances



$$R_{eq} = R_1 + R_2 + \cdots + R_n.$$


Stolen from Wikipedia

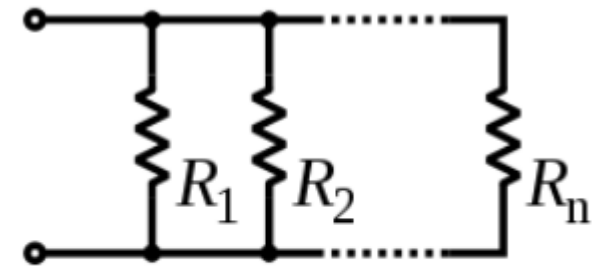


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_n}.$$

Capacitor

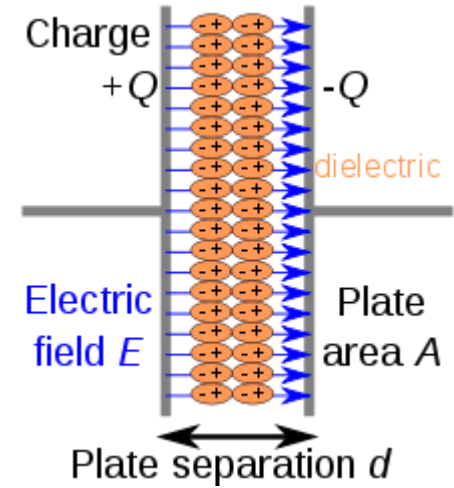
- Stores charges
 - Analogy: Miniature battery
- Value of capacitor measured in Farads [F]
- Reactive
 - Acts as a lossless resistor for alternating currents
 - Measured in Ohms
 - $X = 1/(2\pi f C)$ [Ω]
 - Reactance [Ω] = $1/(2\pi * \text{frequency} * \text{Capacitance})$



Stolen from Wikipedia

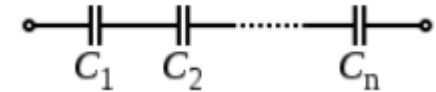

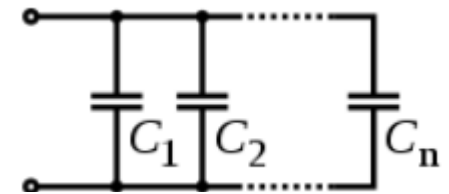
$$\frac{1}{C_{eq}} = \sum_i \frac{1}{C_i} = \frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_n}$$




$$C_{eq} = \sum_i C_i = C_1 + C_2 + \cdots + C_n$$

Inductor

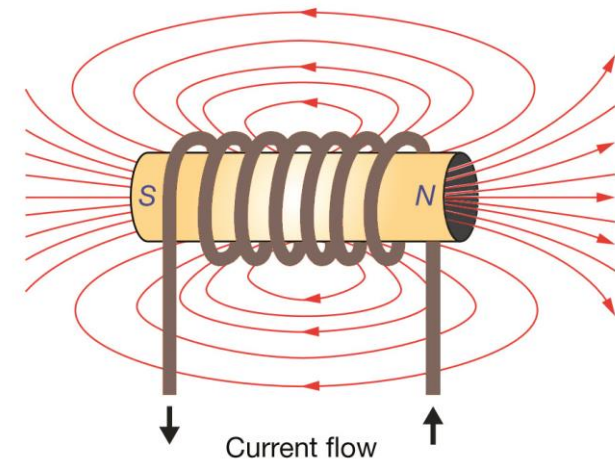
- Stores energy in a magnetic field
 - Inverse of a capacitor
- Value of inductor measured in Henry [H]
- Reactive
 - $X = 2\pi f L$ [Ω]
 - Reactance = 2π * frequency * Inductance



Stolen from Wikipedia

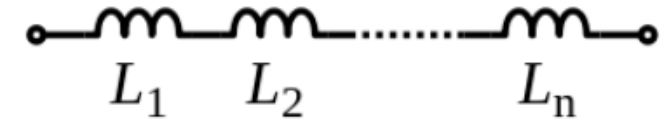

$$L_{eq} = L_1 + L_2 + \dots + L_n$$

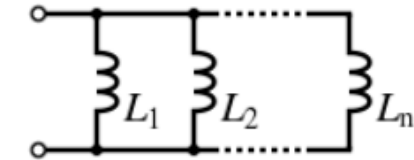


$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$

Impedance

- Complex number
 - Resistance [real]
 - Reactance [imaginary]
 - $Z = R + jX$ [Polar form]
- Frequency dependent
 - Reactance can become dominant for high frequencies
- Ohms law can still be used


Kirchhoff's laws

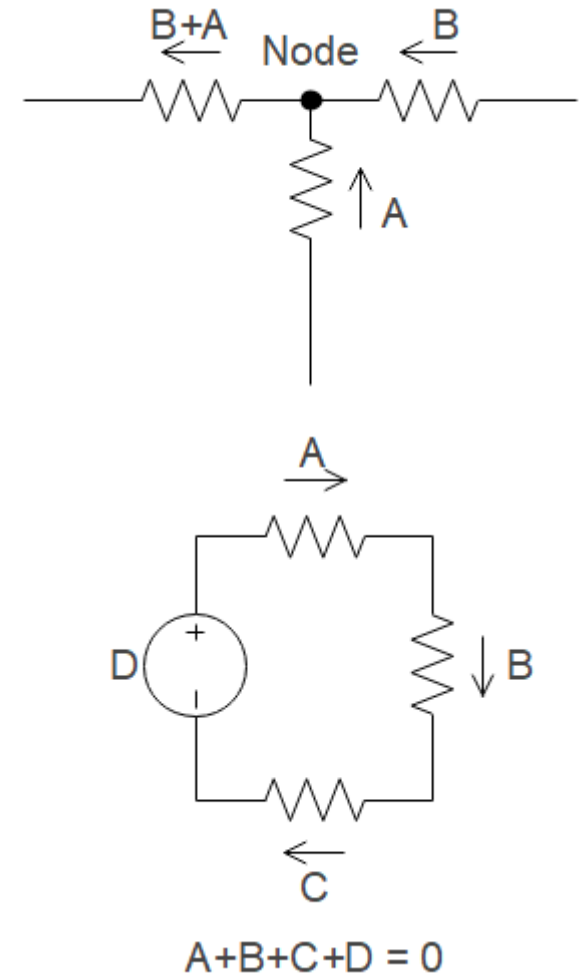- Current law
 - Sum of currents flowing into a node is equal to the sum of currents flowing out
 - Conservation of current – Current can't disappear
- Voltage law
 - Sum of voltages for any closed loop is zero
 - Conservation of potential – Voltages can't disappear



Using Kirchhoff and Ohm's laws

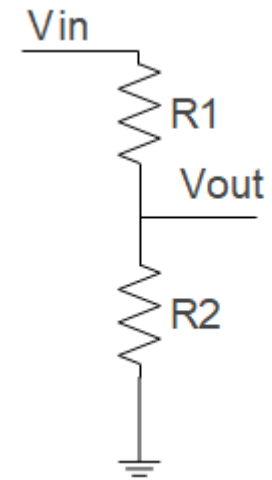
- Voltage law
 - Voltage over R1 and R2 must be equal to V_{in}
- Current law
 - Assuming no current flows out of V_{out}
 - Current through R1 and R2 must be the same
- Ohm's law
 - $V = I * R$
 - $I = V_{in} / (R1 + R2)$
 - $V_{out} = V_{R2} = I * R2$
 $V_{out} = V_{in} / (R1 + R2) * R2$
 $V_{out} = (R2 / (R1 + R2)) * V_{in}$
- This circuit is called a voltage divider



$$V_{out} = (R2 / (R1 + R2)) V_{in}$$


Sanity Check

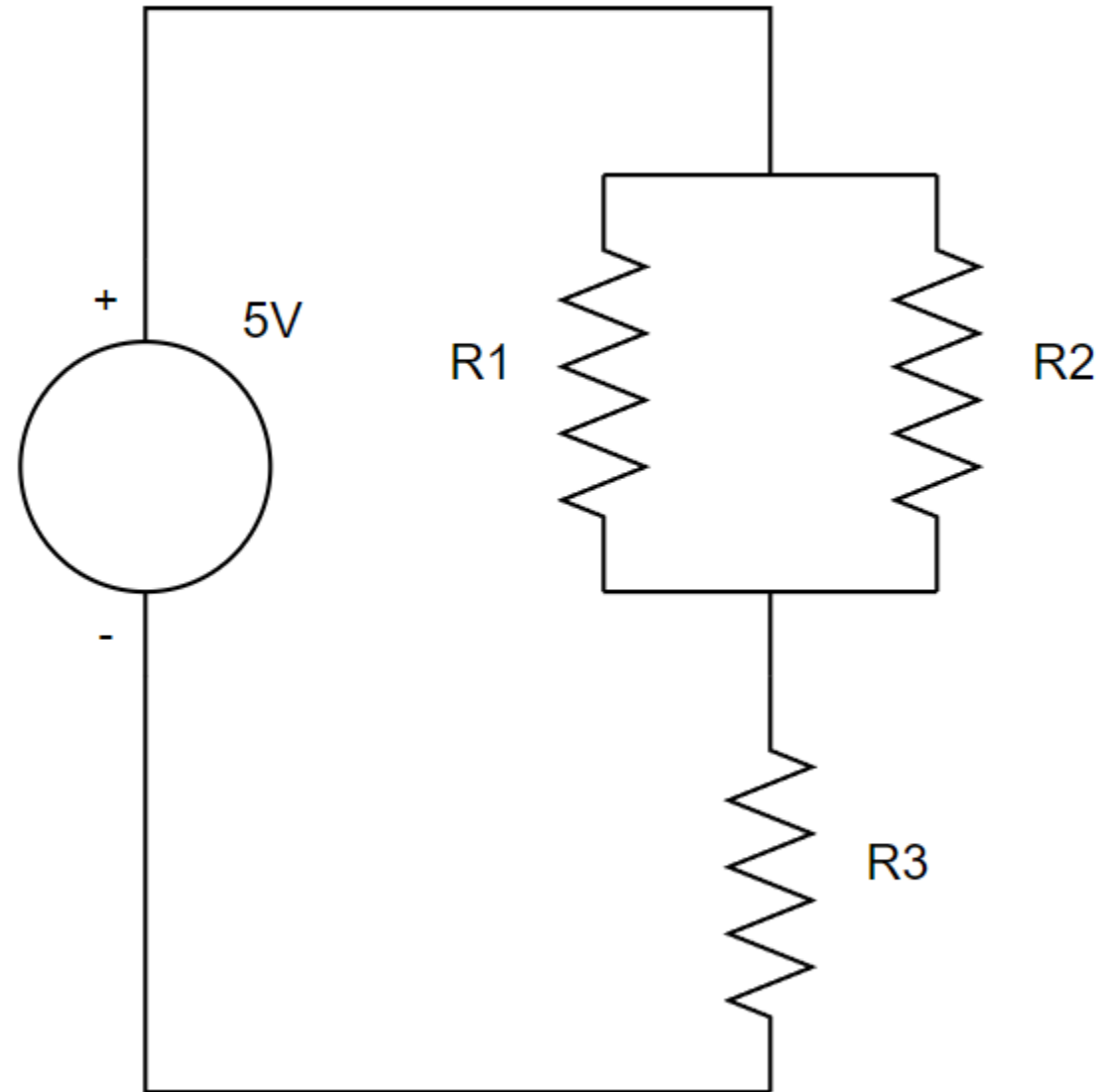- $R1 = R2 = 220\ \Omega$
- $R3 = 110\ \Omega$
- What is the
 - Voltage over $R3$?
 - Current through $R3$?
 - Current through $R1$
- Solution on next slide




Solution

- Voltage over R3?
 - We know
 - $R1 = R2 = 220\ \Omega$
 - $R3 = 110\ \Omega$
 - Equivalent parallel resistance of $R1 \parallel R2 = 110\ \Omega$
 - We can now use the voltage divider formula to get 2.5 V over R3
- Current through R3?
 - Equivalent series resistance of $(R1 \parallel R2) + R3 = 220\ \Omega$
 - Current law: Current into node = current out of node
 - $I_{(R1 \parallel R2)} = I_{R3}$
 - Ohm's law
 - $V = I * R \Rightarrow I = V/R = 5 / 220 = 22.7\ \text{mA}$
- Current through R1?
 - Same resistance for R1 and R2 means current is split equally between both resistors
 - Current law: $I_{(R1 \parallel R2)} = I_{R3}$
 - $I_{R1} = I_{R3} / 2 = 11.35\ \text{mA}$

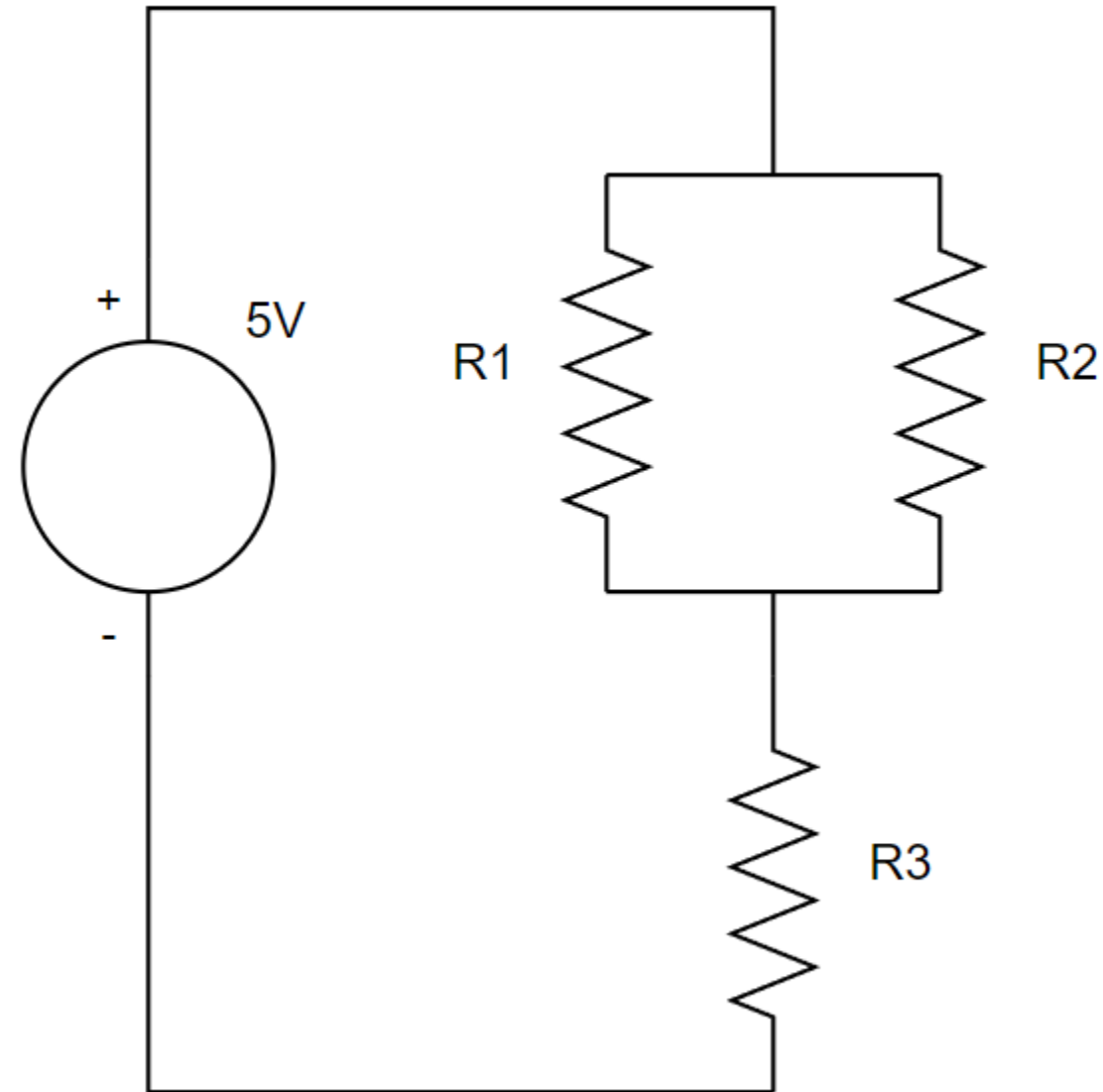

Sanity Check

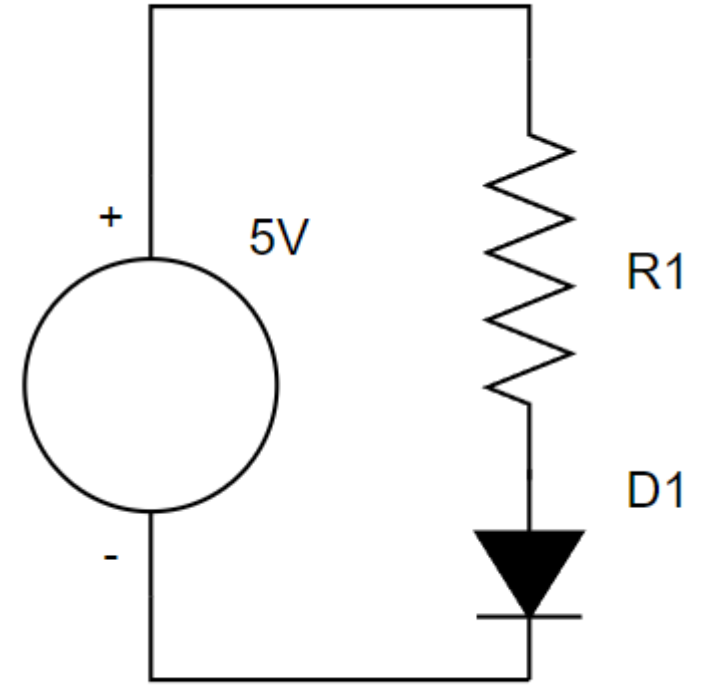- $R1 = 1\text{k}\Omega$
- D1 has a voltage drop of 2 V
- What is the current through the diode D1?
- Solution next slide



Sanity Check

- What is the current through the diode D1?
 - Voltage drop over D1 = 2 V
 - Voltage law: $5\text{ V} = V_{R1} + V_{D1}$
 - Voltage over R1 must be $5 - 2 = 3\text{ V}$
 - Current law: Current through R1 and D1 must be equal
 - $I_{R1} = I_{D1}$
 - Ohm's law: $V = I * R$
 - $V_{R1} = I_{R1} * R1$
 - $I_{R1} = I_{D1} = V_{R1} / R1 = 3/1000 = 3\text{ mA}$

